## 36 Smith Chart and VSWR

• Consider the general phasor expressions

$$V(d) = V^+ e^{j\beta d} (1 + \Gamma_L e^{-j2\beta d})$$
 and  $I(d) = \frac{V^+ e^{j\beta d} (1 - \Gamma_L e^{-j2\beta d})}{Z_o}$ 

describing the voltage and current variations on TL's in sinusoidal steady-state.

- Unless  $\Gamma_L = 0$ , these phasors contain reflected components, which means that voltage and current variations on the line "contain" standing waves.

In that case the phasors go through cycles of magnitude variations as a function of d, and in the voltage magnitude in particular (see margin) varying as

$$|V(d)| = |V^+||1 + \Gamma_L e^{-j2\beta d}| = |V^+||1 + \Gamma(d)$$

takes maximum and minimum values of

$$|V(d)|_{max} = |V^+|(1+|\Gamma_L|)$$
 and  $|V(d)|_{min} = |V^+|(1-|\Gamma_L|)$ 

at locations  $d = d_{max}$  and  $d_{min}$  such that

$$\Gamma(d_{max}) = \Gamma_L e^{-j2\beta d_{max}} = |\Gamma_L|$$
 and  $\Gamma(d_{min}) = \Gamma_L e^{-j2\beta d_{min}} = -|\Gamma_L|$ ,

and

$$d_{max} - d_{min}$$
 is an odd multiple of  $\frac{\lambda}{4}$ 



Complex addition displayed graphically superposed on a Smith Chart



 $|1 + \Gamma(d)|$  minimizes for  $d = d_{min}$ such that  $\Gamma(d_{min}) = -\Gamma(d_{max})$ 

1

- These results can be most easily understood and verified graphically on a SC as shown in the margin.
- We define a parameter known as **voltage standing wave ratio**, or **VSWR** for short, by

$$VSWR \equiv \frac{|V(d_{max})|}{|V(d_{min})|} = \frac{1+|\Gamma_L|}{1-|\Gamma_L|} \quad \Leftrightarrow \quad |\Gamma_L| = \frac{VSWR-1}{VSWR+1}.$$

Notice that the VSWR and  $|\Gamma_L|$  form a **bilinear transform pair** just like

$$z = \frac{1+\Gamma}{1-\Gamma} \quad \Leftrightarrow \quad \Gamma = \frac{z-1}{z+1}.$$

Since

$$\Gamma(d_{max}) = |\Gamma_L| \implies \text{VSWR} = \frac{1 + \Gamma(d_{max})}{1 - \Gamma(d_{max})}$$

this analogy between the transform pairs also implies that

$$z(d_{max}) = \text{VSWR},$$

as explicitly marked on the the SC shown in the margin . Consequently,

- the VSWR of any TL can be directly read off from its SC plot as the normalized impedance value  $z(d_{max})$  on constant- $|\Gamma_L|$  circle crossing the positive real axis of the complex plane.



Complex addition displayed graphically superposed on a Smith Chart



 $<sup>|1 + \</sup>Gamma(d)|$  minimizes for  $d = d_{min}$ such that  $\Gamma(d_{min}) = -\Gamma(d_{max})$ 

- The extreme values the VSWR can take are:
  - 1. VSWR=1 if  $|\Gamma_L| = 0$  and the TL carries no reflected wave.
  - 2. VSWR= $\infty$  if  $|\Gamma_L| = 1$  corresponding to having a short, open, or a purely reactive load that causes a total reflection.



- In the lab it is easy and useful to determine the VSWR and  $d_{max}$  or  $d_{min}$  of a TL circuit with an unknown load, since
- 1. given the VSWR,

$$|\Gamma_L| = \frac{\text{VSWR} - 1}{\text{VSWR} + 1}$$

is easily determined, and

- 2. given  $d_{max}$  or  $d_{min}$  the complex  $\Gamma_L$  or its transform  $z_L$  can be easily obtained.
- Say  $d_{max}$  is known: then,
  - since (as we have seen above)

$$\Gamma(d_{max}) = \Gamma_L e^{-j2\beta d_{max}} = |\Gamma_L|$$

it follows that

$$\Gamma_L = |\Gamma_L| e^{j2\beta d_{max}} \quad \Rightarrow \quad z_L = \frac{1+\Gamma_L}{1-\Gamma_L}$$

• alternatively,  $z_L$  can be obtained directly on the SC by rotating counterclockwise by  $d_{max}$  from the location of

$$z(d_{max}) = \text{VSWR}$$

These techniques are illustrated in the next example.

4



Complex addition displayed graphically superposed on a Smith Chart



 $|1 + \Gamma(d)|$  maximizes for  $d = d_{max}$ 

 $|1 + \Gamma(d)|$  minimizes for  $d = d_{min}$ such that  $\Gamma(d_{min}) = -\Gamma(d_{max})$  **Example 1:** An unknown load  $Z_L$  on a  $Z_o = 50 \Omega$  TL has

 $V(d_{min}) = 20 \text{ V}, \quad , d_{min} = 0.125\lambda \text{ and VSWR} = 4.$ 

Determine (a) the load impedance  $Z_L$ , and (b) the average power  $P_L$  absorbed by the load.

## Solution:

(a) As shown in the top SC in the margin, VSWR=4 is entered in the SC as  $z(d_{max}) = 4 + j0$ , and constant  $|\Gamma_L|$  circle is then drawn (red circle) passing through  $z(d_{max}) = 4$ .

Right across  $z(d_{max}) = 4$  on the circle is  $z(d_{min}) = 0.25$ .

A counter-clockwise rotation from  $z(d_{min}) = 0.25$  by one fourth of a full circle corresponding to a displacement of  $d_{min} = 0.125\lambda$  (a full circle corresponds to a  $\lambda/2$  displacement) takes us to

 $z_L \approx 0.4706 - j0.8823$ 

as shown in the second SC. Hence, this gives

$$Z_L = Z_o z_L = 50(0.4706 - j0.8823) = 23.53 - j44.12\,\Omega$$

(b) We will calculate  $P_L$  by using  $V(d_{min})$  and  $I(d_{min})$ . Since

 $z(d_{min}) = 0.25$  it follows that  $Z(d_{min}) = \frac{1}{4}50 \,\Omega = 12.5 \,\Omega.$ 



Therefore the voltage and current phasors at the voltage minimum location are

$$V(d_{min}) = 20 \,\mathrm{V}$$
 and  $I(d_{min}) = \frac{20 \,\mathrm{V}}{12.5 \,\Omega}.$ 

Average power transported toward the load at  $d - d_{min}$  is, therefore,

$$P(d_{min}) = \frac{1}{2} \operatorname{Re}\{V(d_{min})I(d_{min})^*\} = \frac{1}{2} \operatorname{Re}\{20\frac{20}{12.5}\} = \frac{400}{25} \operatorname{W} = 16 \operatorname{W}.$$

Since the TL is assumed to be lossless we should have

$$P_L = P(d_{min}) = 16 \,\mathrm{W}.$$



**Example 2:** If the TL circuit in Example 1 has  $l = 0.625\lambda$ , and a generator with an internal impedance  $Z_g = 50 \Omega$ , determine the generator voltage  $V_g$ .

**Solution:** Given that  $l = 0.625\lambda$  and  $d_{min} = 0.125\lambda$ , we note that there is just one half-wave transformer between  $l = 0.625\lambda$  and  $d_{min} = 0.125\lambda$ . Therefore

$$V_{in} = -V(d_{min}) = -20 \,\mathrm{V}$$
 and  $Z_{in} = Z(d_{min}) = 12.5 \,\Omega$ .

But also

$$V_{in} = V_g \frac{Z_{in}}{Z_g + Z_{in}}.$$

Consequently,

$$V_g = V_{in} \frac{Z_g + Z_{in}}{Z_{in}} = -20 \frac{50 + 12.5}{12.5} = -20 \frac{62.5}{12.5} = -100 \,\mathrm{V}.$$

**Example 3:** Determine  $V^+$  and  $V^-$  in the circuit of Examples 1 and 2 above such that the voltage phasor on the line is given by

$$V(d) = V^+ e^{j\beta d} + V^- e^{-j\beta d}.$$

Solution: Looking back to Example 1 (also see the SC's in the margin), we first note that

$$|\Gamma_L| = \frac{\text{VSWR} - 1}{\text{VSWR} + 1} = \frac{4 - 1}{4 + 1} = 0.6 = \Gamma(d_{max}) = -\Gamma(d_{min}).$$

Hence, evaluating V(d) at  $d = d_{min}$ , we have

$$V(d_{min}) = V^+ e^{j\beta d_{min}} (1 + \Gamma(d_{min}))$$
  
=  $V^+ (e^{j\frac{2\pi}{\lambda}\frac{\lambda}{8}}) (1 + (-0.6)) = 0.4 e^{j\frac{\pi}{4}} V^+ = 20 \text{ V},$ 

from which

$$V^+ = 50e^{-j\frac{\pi}{4}}$$
 V.

Since

$$\Gamma_L = \Gamma(0) = \Gamma(d_{min})e^{j2\beta d_{min}} = -0.6e^{j\frac{\pi}{2}},$$

it follows that

$$V^{-} = \Gamma_L V^{+} = -0.6e^{j\frac{\pi}{2}} \times 50e^{-j\frac{\pi}{4}} = -30e^{j\frac{\pi}{4}} \mathrm{V}.$$



**Example 4:** Determine the load current  $I_L = I(0) V^+$  in the circuit of Examples 1-3 above.

 ${\bf Solution:} \ {\rm In \ general},$ 

$$I(d) = \frac{V^+ e^{j\beta d} - V^- e^{-j\beta d}}{Z_o}.$$

Therefore,

$$I_L = I(0) = \frac{V^+ - V^-}{Z_o}.$$

Using  $Z_o = 50 \Omega$  and

$$V^+ = 50e^{-j\frac{\pi}{4}}V$$
 and  $V^- = -30e^{j\frac{\pi}{4}}V$ 

from Example 3, we find that

$$I_L = \frac{50e^{-j\frac{\pi}{4}} + 30e^{j\frac{\pi}{4}}}{50} = e^{-j\frac{\pi}{4}} + 0.6e^{j\frac{\pi}{4}} \,\mathrm{A}.$$

