

38 Equivalent circuit models of coupled antennas

- Since Maxwell's equations and the associated boundary conditions which govern the interaction of a pair of antennas with input currents $I_{1,2}$ and response voltages $V_{1,2}$ are **linear**, the *equivalent circuit model* describing the relationships of $I_{1,2}$ and $V_{1,2}$ is also **linear** and obeys a set of equations



$$\begin{aligned} V_1 &= Z_1 I_1 + Z_{12} I_2 \\ V_2 &= Z_{21} I_1 + Z_2 I_2. \end{aligned}$$

- With I_2 set to zero, we recognize Z_1 above as the input impedance of ant.-1, while Z_{21} is a coupling impedance connecting the open circuit response voltage of ant.2 to the driver current of ant.1.
- Likewise, Z_2 is the input impedance of ant.2 and Z_{12} is a coupling impedance from ant.2 to ant.1.

- The reciprocal behaviour of a pair of antennas separated in free space restricts the coupling impedances in the model circuit to satisfy

$$Z_{21} \equiv \frac{V_2}{I_1} \Big|_{I_2=0} = Z_{12} \equiv \frac{V_1}{I_2} \Big|_{I_1=0} \equiv Z_c$$

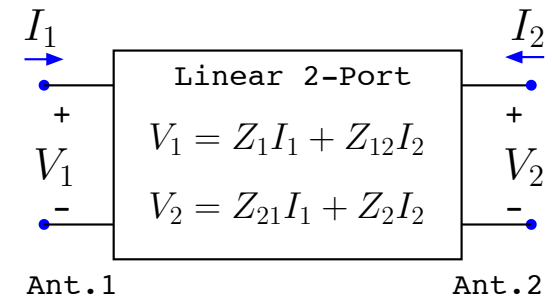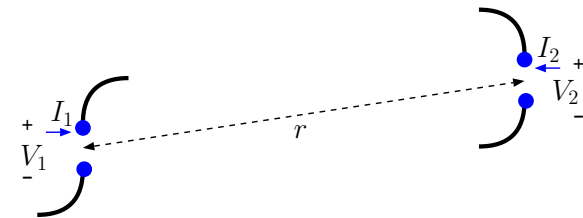so that transmission gain P_t/P_r is independent of the transmission and reception roles assigned to the antennas (as verified below).



With that restriction the equivalent circuit model of the coupling simplifies as (see margin)

$$\begin{aligned} V_1 &= Z_1 I_1 + Z_c I_2 \\ V_2 &= Z_c I_1 + Z_2 I_2. \end{aligned}$$

- With reference to the circuit diagram in the margin, note that the open circuit voltage at ant.2 terminals is

$$V_2 = I_1 Z_c \equiv V_T,$$

while the Thevenin impedance seen from ant.2 terminals is (using the source suppression method where $I_1 = 0$ case is considered)

$$Z_T = Z_2.$$

Therefore, the Thevenin equivalent circuit of ant.2 during reception takes the form shown in the margin.


- From the Thevenin equivalent we identify the average power transferred by I_1 to a possible matched termination of ant.2 as

$$P_r = \frac{|V_T|^2}{8\text{Re}\{Z_T\}} = \frac{|I_1|^2 |Z_c|^2}{8\text{Re}\{Z_2\}}.$$


- To calculate the transmitted power P_t of ant.1 when ant.2 is terminated by matched $Z_L = Z_2^*$ (see margin), we first note that

$$V_1 \approx I_1 Z_1$$

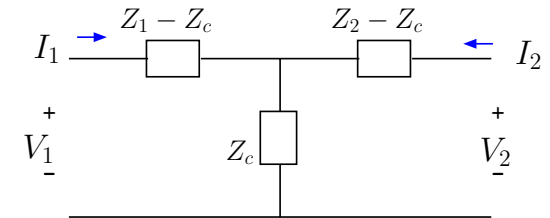Reciprocal circuit model for antenna coupling:



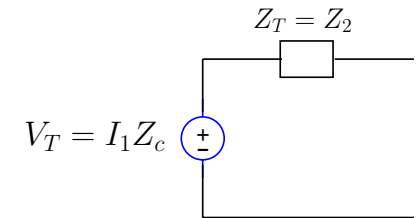Thevenin equivalent circuit of ant.2 in reception:



if $|Z_c| \ll |Z_1|$, in which case ant.1 has a power input

$$P_t = \frac{1}{2} \text{Re}\{V_1 I_1^*\} \approx \frac{1}{2} |I_1|^2 \text{Re}\{Z_1\}.$$

The above expressions can be combined as

$$P_r \approx \frac{1}{2} |I_1|^2 \text{Re}\{Z_1\} \frac{|Z_c|^2}{4 \text{Re}\{Z_1\} \text{Re}\{Z_2\}} = P_t \frac{|Z_c|^2}{4 \text{Re}\{Z_1\} \text{Re}\{Z_2\}},$$

which is a reciprocal relation symmetric in Z_1 and Z_2 , mimicking the symmetry of Friis transmission formula with respect to G_1 and G_2 , such that


$$\frac{|Z_c|^2}{4 \text{Re}\{Z_1\} \text{Re}\{Z_2\}} = \frac{\lambda^2 G_1 G_2}{(4\pi r)^2} \Rightarrow |Z_c|^2 = \frac{G_1 \text{Re}\{Z_1\} G_2 \text{Re}\{Z_2\}}{(2\pi r/\lambda)^2}$$

is implied. As shown in HW, the exact calculation of P_r , without making use of $|Z_c| \ll |Z_1|$, yields

$$P_r = P_t \frac{|Z_c|^2}{4 \text{Re}\{Z_1\} \text{Re}\{Z_2\} - 2 \text{Re}\{Z_c^2\}}.$$

- The above reciprocal circuit model describes the behavior of coupled antennas (of any type) separated in free space. It also applies with antennas embedded in material media (even with inhomogeneous μ , ϵ , and σ) so long as the medium is isotropic and linear as shown directly from a reciprocity condition derived from Maxwell's equations (see ECE 454 and 520). Applications of non-reciprocal antenna coupling in anisotropic media are treated in ECE 458.

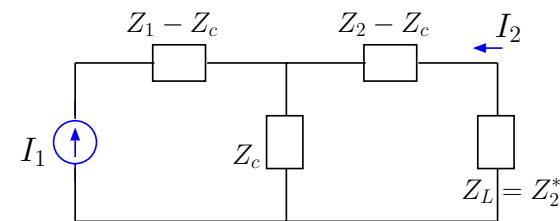Eqv. ckt. showing ant.1 in transmission and ant.2 in reception with matched load:



Note that the coupling impedance Z_c gets weaker with increasing r/λ and gets getting stronger with the product of antenna gains G_1 and G_2 .

This model for Z_c and the Friis transmission formula are only valid when the antennas are placed within the far-fields (Fraunhofer region) of each other.

Example 1: Consider a \hat{z} -polarized half-wave dipole antenna with an input impedance of $Z_2 = 73 \Omega$ located at the origin. Determine the time-average power received by the antenna if it has a matched termination and the incident field has an electric field phasor

$$\tilde{\mathbf{E}}_{inc} = 120\pi \hat{z} e^{j2\pi x} \text{ V/m.}$$

Solution: The incident field has a wave vector

$$\mathbf{k} = -2\pi \hat{x} \text{ rad/m,}$$

indicating the antenna sees the incident wave coming from direction $\theta = 90^\circ$ with a polarization direction $\hat{\theta}$. Since

$$\lambda = \frac{2\pi}{k} = \frac{2\pi}{|\mathbf{k}|} = \frac{2\pi}{2\pi} = 1 \text{ m}$$

and

$$A(\theta, \phi) = \frac{\lambda^2}{4\pi} G(90^\circ, \phi) = \frac{1}{4\pi} \underbrace{(1.64)}_{\text{half-wave-dipole gain at } 90^\circ} = \frac{1.64}{4\pi} \text{ m}^2,$$

and, furthermore,

$$S_{inc} = \frac{|\tilde{\mathbf{E}}_{inc}|^2}{2\eta} = \frac{(120\pi)^2}{2 \times 120\pi} = 60\pi \text{ W/m}^2,$$

it follows that

$$P_r = S_{inc} A(\theta, \phi) = 60\pi \times \frac{1.64}{4\pi} = 24.6 \text{ W}$$

is the time-averaged power received by the antenna with the matched termination.

Example 2: Repeat Example 1 if the antenna is terminated by $Z_L = 36.5 \Omega$. Also find the antenna open circuit voltage V_T .

Solution: In this case power received will be less than the available power

$$P_r = S_{inc}A(\theta, \phi) = 60\pi \times \frac{1.64}{4\pi} = 24.6 \text{ W}$$

of the antenna obtained in Example 1.

Since the the available power of an antenna with an input impedance of Z_2 is necessarily

$$P_r = \frac{|V_T|^2}{8\text{Re}\{Z_2\}}$$

in terms of the antenna open-circuit voltage phasor V_T , we obtain, using $P_r = 24.6$ W and $Z_2 = 73 \Omega$,

$$|V_T| = \sqrt{8\text{Re}\{Z_2\}P_r} = 119.86 \text{ V}.$$

Terminating the Thevenin equivalent of the receiving half-dipole consisting of V_T and $Z_2 = 73 \Omega$ in series with $Z_L = 36.5 \Omega$, we deduce a load current of

$$I_L = \frac{V_T}{Z_2 + Z_L}.$$

Therefore, the load voltage is

$$V_L = I_L Z_L = \frac{V_T Z_L}{Z_2 + Z_L},$$

and the average load power is

$$\begin{aligned} P_L &= \frac{1}{2} \text{Re}\{V_L I_L^*\} = \frac{|V_T|^2 \text{Re}\{Z_L\}}{2|Z_2 + Z_L|^2} = \frac{|V_T|^2}{8\text{Re}\{Z_2\}} \frac{4\text{Re}\{Z_2\}\text{Re}\{Z_L\}}{|Z_2 + Z_L|^2} \\ &= P_r \frac{4\text{Re}\{Z_2\}\text{Re}\{Z_L\}}{|Z_2 + Z_L|^2}. \end{aligned}$$

Substituting for P_r, Z_2 , and Z_L , we find

$$P_L = P_r \frac{4\operatorname{Re}\{Z_2\}\operatorname{Re}\{Z_L\}}{|Z_2 + Z_L|^2} = 24.6 \frac{4 \times 73 \times 36.5}{|73 + 36.5|^2} = 24.6 \frac{4 \times 2}{9} = 21.87 \text{ W.}$$